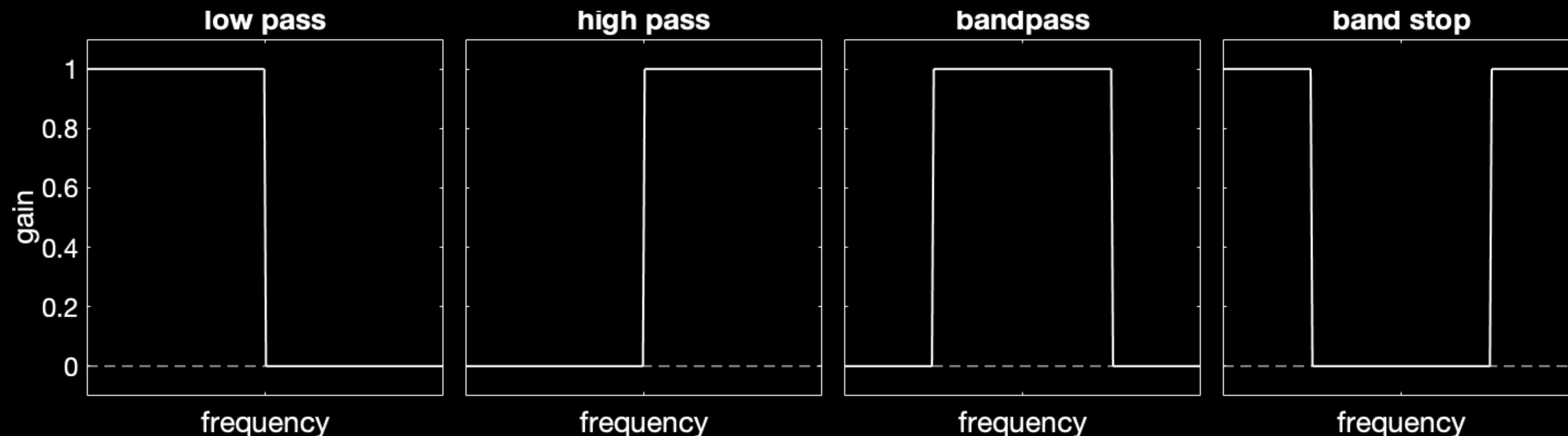


# Filters


- Any time-varying voltage can be expressed as a superposition of sinusoids of different frequencies
- A *filter* removes undesired frequencies
  - Noise (e.g. 60 Hz, high-frequency hiss)
  - Irrelevant frequencies (e.g.  $< 20$  Hz or  $> 20$  kHz for audio) to prevent aliasing
- Types:


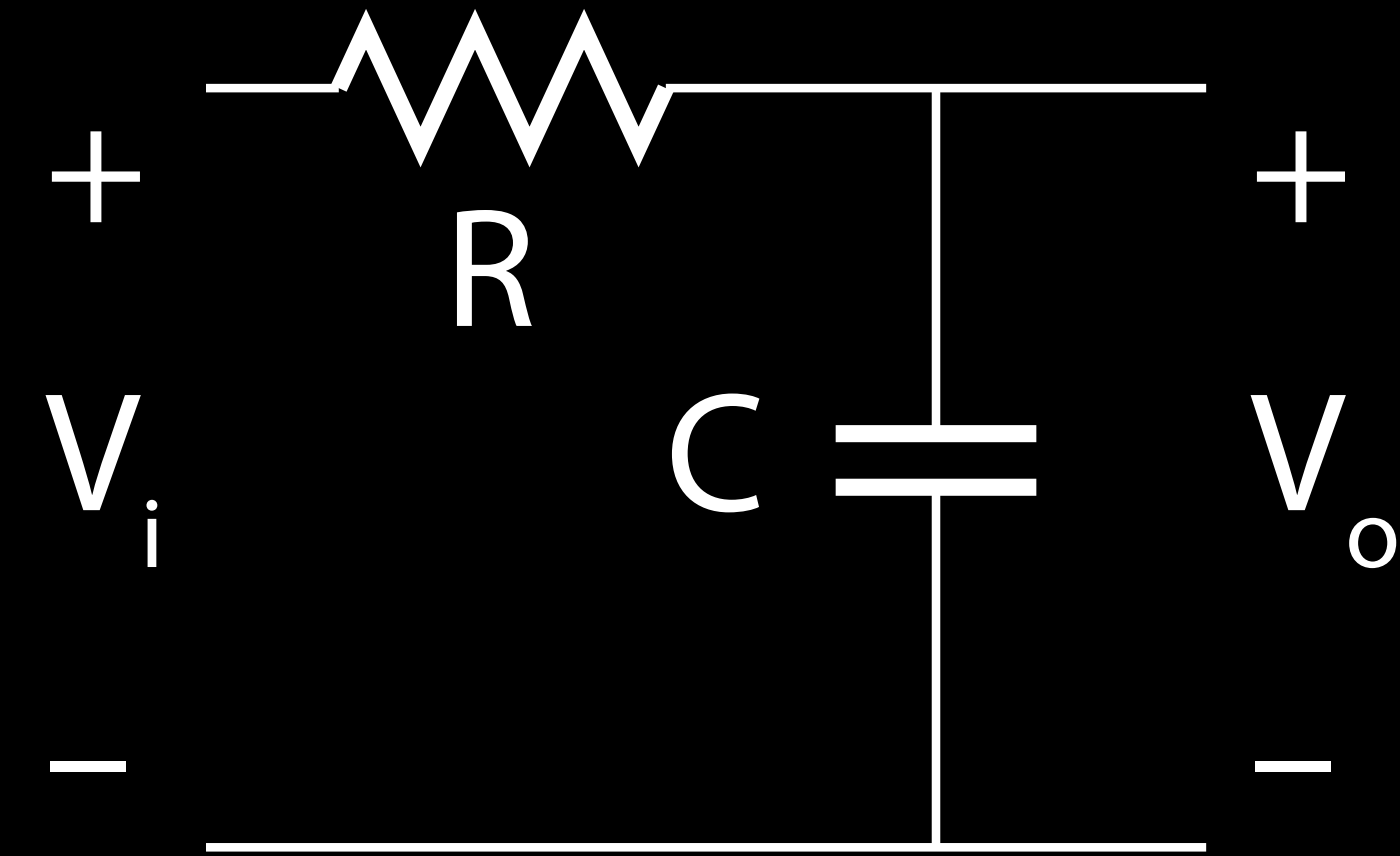
# The simplest low-pass filter

- First-order Butterworth, aka RC
- Voltage law:  $RC \frac{\partial V_o}{\partial t} + V_o = V_i$
- If  $V_i = A \sin \omega t$ , the long-term output is
 
$$V_o = \frac{A}{\sqrt{1 + (RC\omega)^2}} \sin(\omega t - \arctan RC\omega)$$


reduced amplitude
still a sin!
phase shift
- Amplitude of  $V_o$  at frequency  $\omega = 0$ ?  $A$
- Amplitude of  $V_o$  at frequency  $\omega = \infty$ ?  $0$
- Cutoff frequency?  $\frac{1}{RC}$





$$G = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

$$\phi = \arctan RC\omega$$

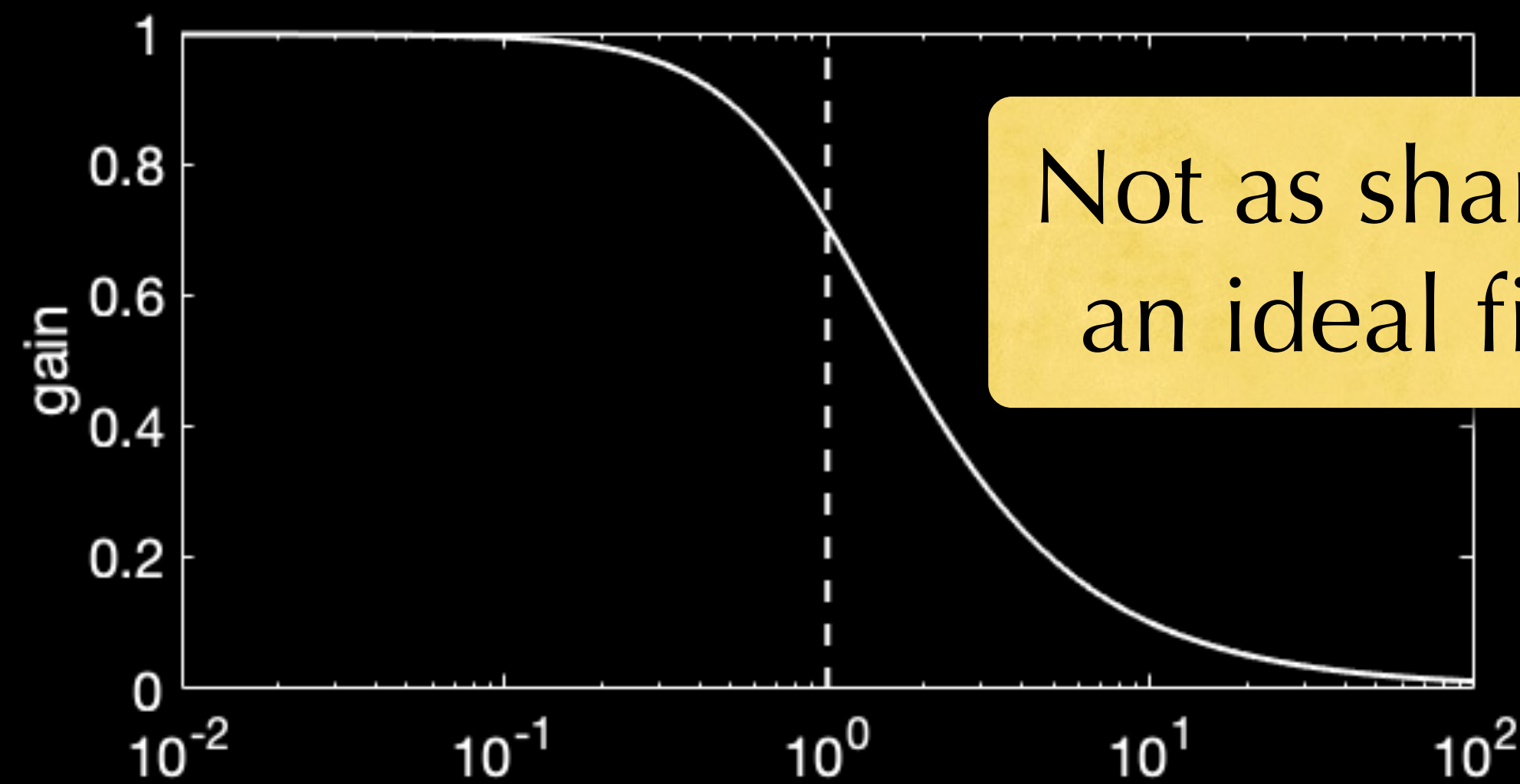
# First-order low-pass Butterworth filter





Not as sharp as  
an ideal filter

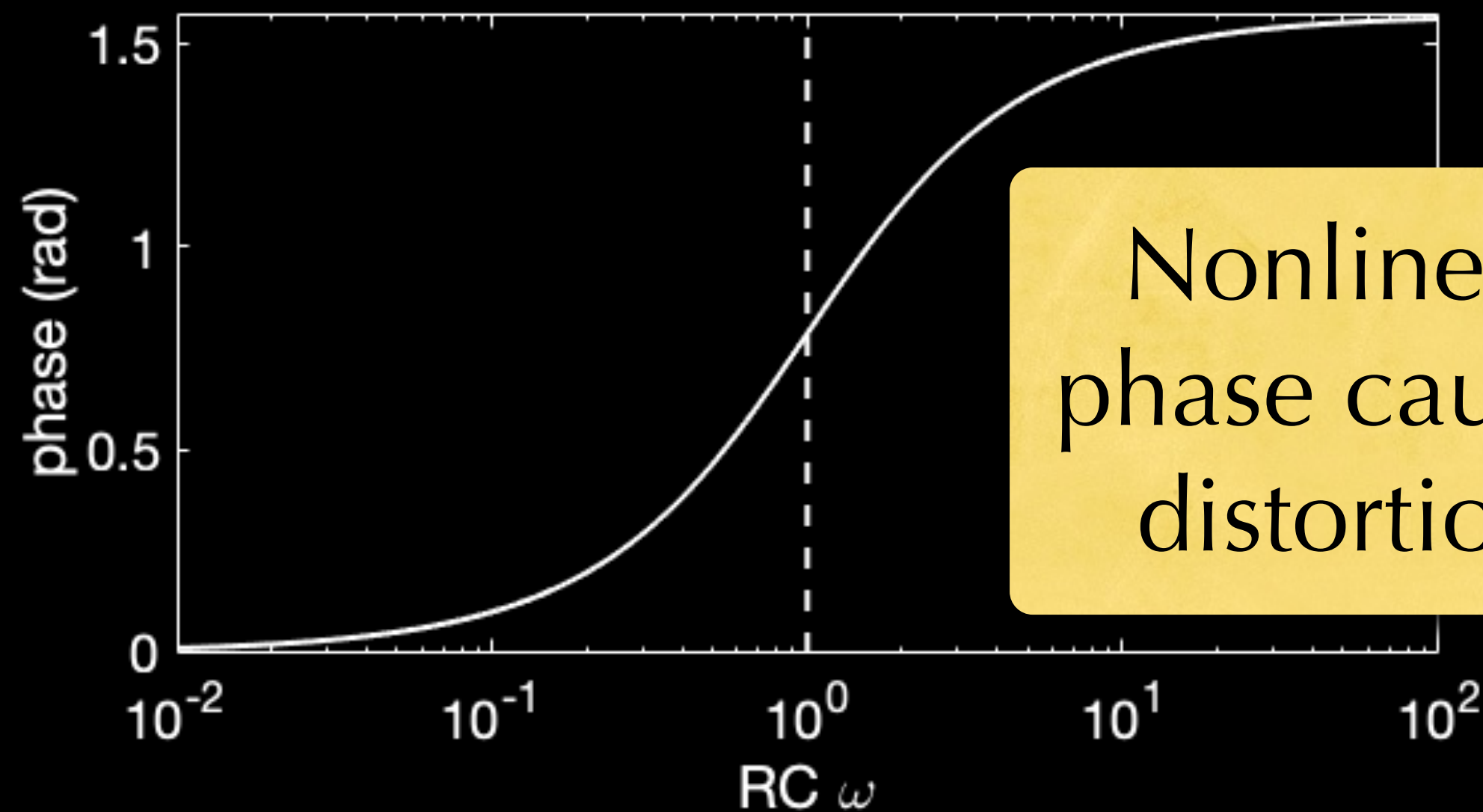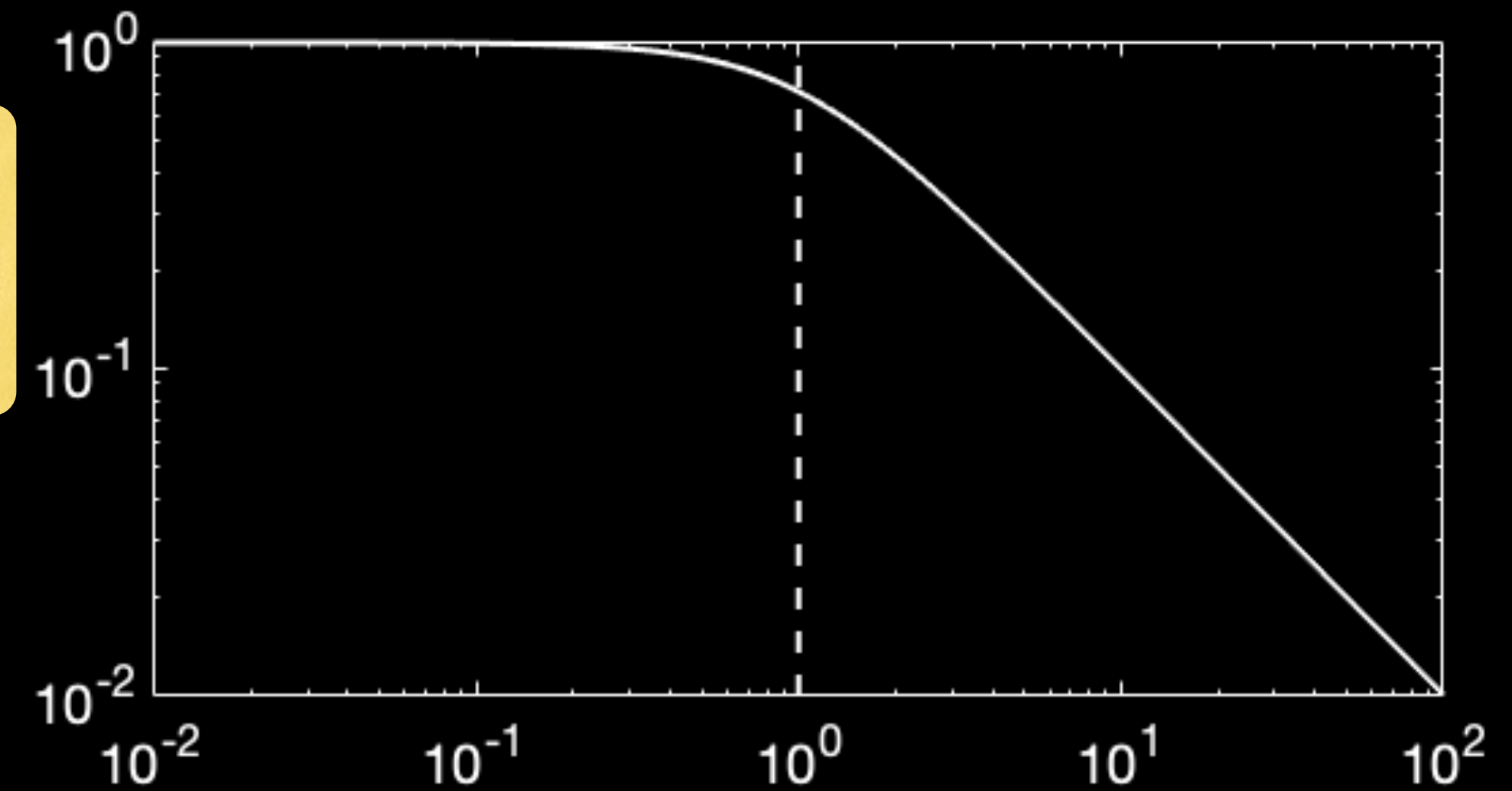

Nonlinear  
phase causes  
distortion

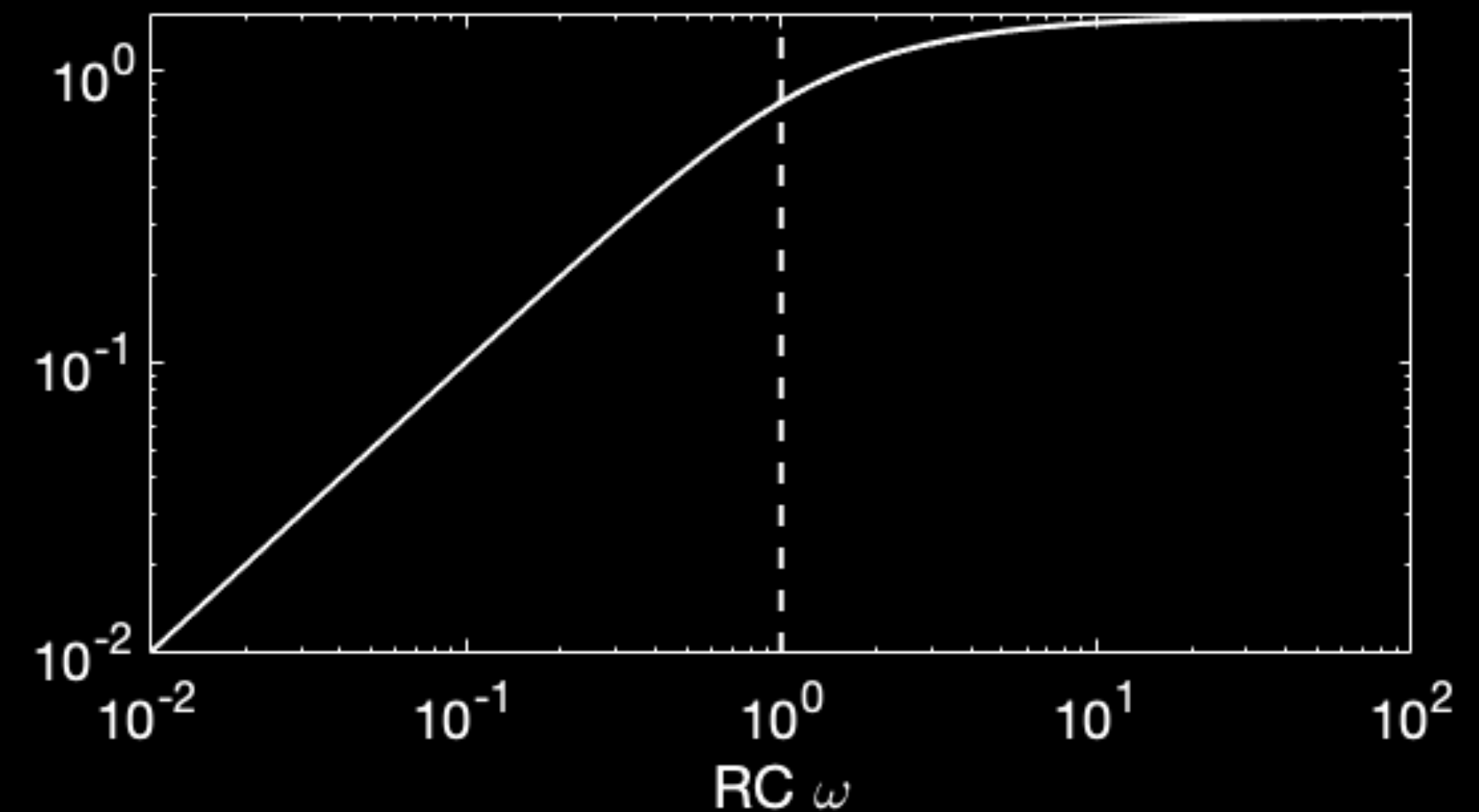


# Low-pass Butterworth filters

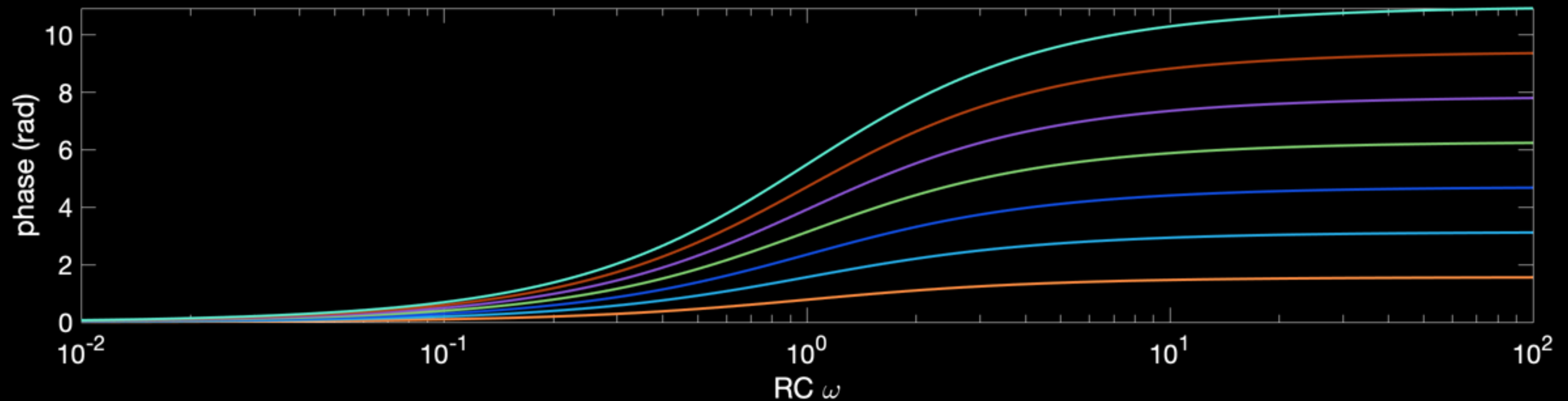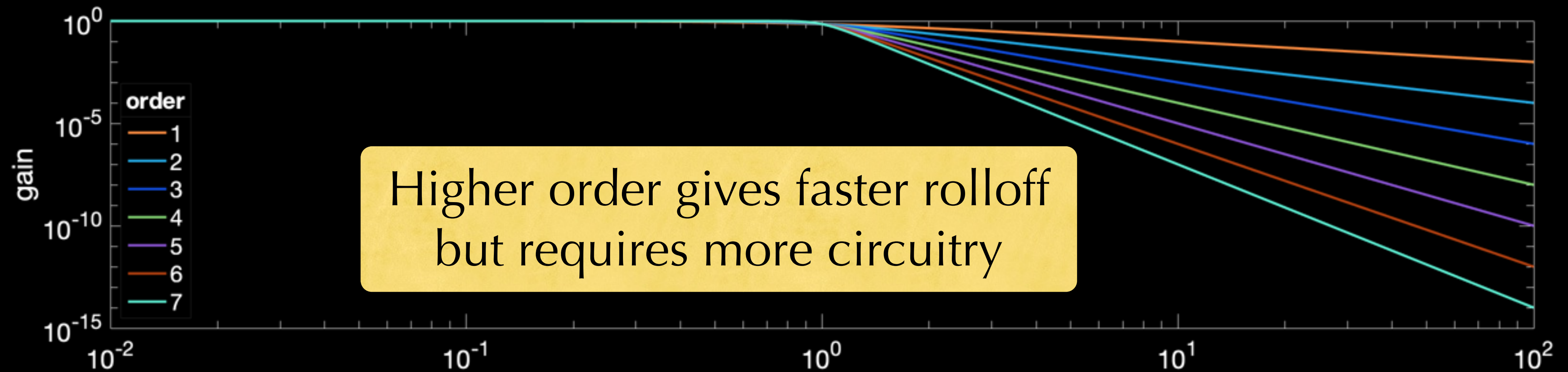
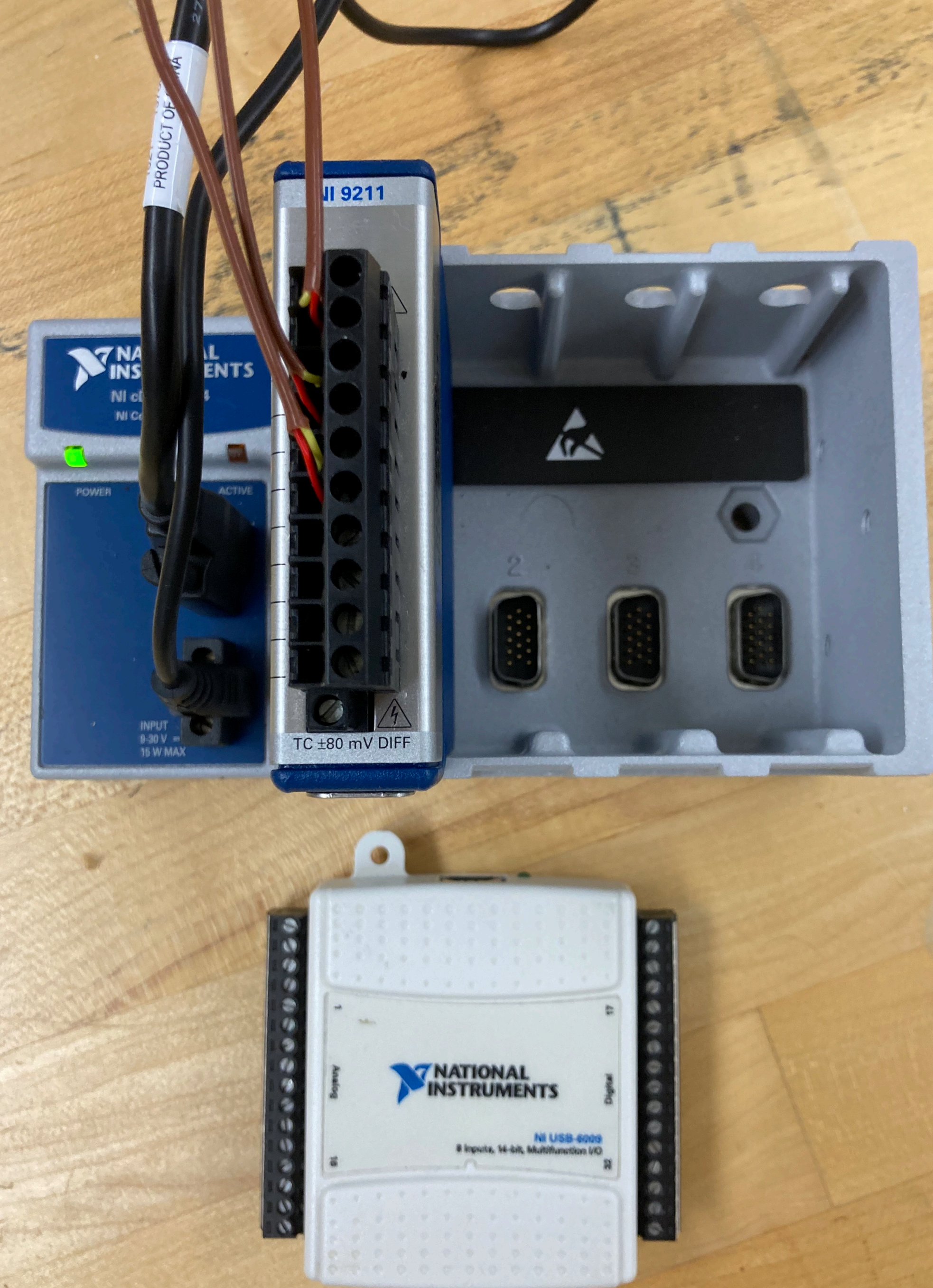
# Computerized data acquisition<sup>28</sup>

- Often connect via USB; sometimes internal
- Wires from transducers connect to screw terminals
- Range often -5 V to 5 V or 0 V to 10 V
- Special ports for thermocouples
- Analog inputs, digital input/output, occasionally analog outputs
- Varying channel count (1 to ~30), bit depth (8, 12, 16), sampling rates ( $\sim 1$  to  $\sim 10^6$  S/s)
- Software interface (LabView, Matlab, ...)
- National Instruments, Measurement Computing, Keyence, Arduino, ...



# Writing a Methods section

Explain what you did so that an engineer could repeat your work.

- Post the question(s) being addressed
- State the data you used to answer this question, explaining why this data is appropriate to answer it
- Explain the experimental setup and how you made it
- Explain process of data collection
- Explain how you analyzed the data